



VERILOG LAB1

DIGITAL VERIFICATION




NAME	OMNIA MOHAMED SELIM
------	---------------------

Table of Contents

Mux4-1 using mux2-1	2
Simulation results.....	2
Up-down 4-bit counter.....	2
Design code	2
Simulation results.....	2
Example3.....	3
Design code	3
Simulation results.....	3
Example4: design logic circuit for the truth table	4
Design code	4
Simulation results.....	4
+ve edge detector	4
Design code	4
Simulation results.....	4
4-bit PISO	5
Design code	5
Simulation results.....	5
4-bit SIPO	5
Design code	5
Simulation results.....	6
N-BIT RING COUNTER.....	6
Design code	6
Simulation results.....	7
ROM	7
Design code	7
Simulation results.....	7
Memory buffer	8
Design code	8
Simulation results.....	8

Simulation results

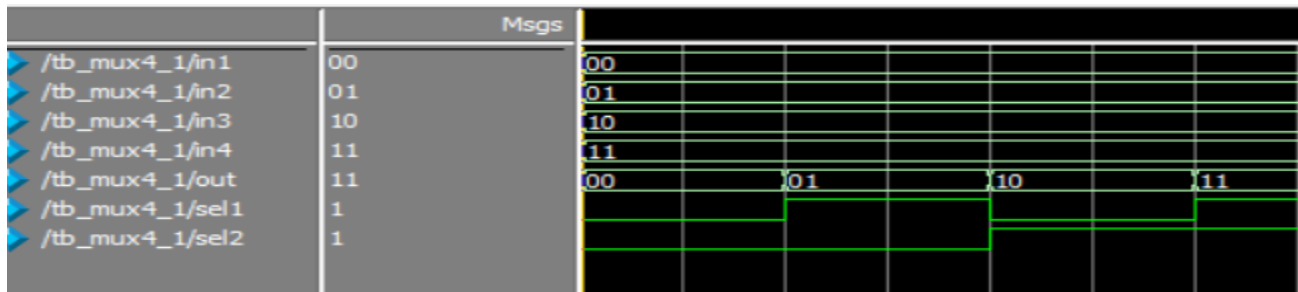

10/11/2016 10:00:00 AM

```
VSIM 126> run
```

```
# in1=00,in2=01,in3=10,in4=11 ,sel1=0,sel2=0 , out=00
# in1=00,in2=01,in3=10,in4=11 ,sel1=1,sel2=0 , out=01
# in1=00,in2=01,in3=10,in4=11 ,sel1=0,sel2=1 , out=10
# in1=00,in2=01,in3=10,in4=11 ,sel1=1,sel2=1 , out=11
```

Up-down 4-bit counter

Design code


```

module updown_counter4(input mode,clk,reset,output reg [3:0] q);

always@(posedge clk) begin
    if(reset==1) q<=0;
    else begin
        if(mode==0) begin //down counter
            if(q !=0) q<=q-1;
            else q<=4'b1111;
        end
        else begin
            if (q!=4'b1111) q<=q+1;
            else q<=0;
        end
    end
end
endmodule

```

Simulation results

 


Example3

Design code

```
module truth_table(input [0:2] s,input e,output reg d0,d1,d2,d3,d4,d5,d6,d7);  
  
always@(*) begin  
  if(e) begin  
    case(s)  
      3'b000: {d0,d1,d2,d3,d4,d5,d6,d7}=8'b0000_0001;  
      3'b001: {d0,d1,d2,d3,d4,d5,d6,d7}=8'b0000_0010;  
      3'b010: {d0,d1,d2,d3,d4,d5,d6,d7}=8'b0000_0100;  
      3'b011: {d0,d1,d2,d3,d4,d5,d6,d7}=8'b0000_1000;  
      3'b100: {d0,d1,d2,d3,d4,d5,d6,d7}=8'b0001_0000;  
      3'b101: {d0,d1,d2,d3,d4,d5,d6,d7}=8'b0010_0000;  
      3'b110: {d0,d1,d2,d3,d4,d5,d6,d7}=8'b0100_0000;  
      3'b111: {d0,d1,d2,d3,d4,d5,d6,d7}=8'b1000_0000;  
    endcase  
  end  
else begin  
  {d0,d1,d2,d3,d4,d5,d6,d7}=8'b0000_0000;  
end  
end  
endmodule
```

Simulation results

```
VSIM 119> run  
# s=xxx,e=0,d0=0,d1=0,d2=0,d3=0,d4=0,d5=0,d6=0,d7=0  
# s=000,e=1,d0=0,d1=0,d2=0,d3=0,d4=0,d5=0,d6=0,d7=1  
# s=001,e=1,d0=0,d1=0,d2=0,d3=0,d4=0,d5=0,d6=1,d7=0  
# s=010,e=1,d0=0,d1=0,d2=0,d3=0,d4=0,d5=1,d6=0,d7=0  
# s=011,e=1,d0=0,d1=0,d2=0,d3=0,d4=1,d5=0,d6=0,d7=0  
# s=100,e=1,d0=0,d1=0,d2=0,d3=1,d4=0,d5=0,d6=0,d7=0  
# s=101,e=1,d0=0,d1=0,d2=1,d3=0,d4=0,d5=0,d6=0,d7=0  
# s=110,e=1,d0=0,d1=1,d2=0,d3=0,d4=0,d5=0,d6=0,d7=0  
# s=111,e=1,d0=1,d1=0,d2=0,d3=0,d4=0,d5=0,d6=0,d7=0
```

 


Example4: design logic circuit for the truth table

Design code

```
module truth4design (input A,B,C,output OUT);  
  assign OUT=(A&B) | (C&B);  
  
endmodule
```

Simulation results

 


```
# A=0,B=0,C=0,OUT=0  
# A=0,B=0,C=1,OUT=0  
# A=0,B=1,C=0,OUT=0  
# A=0,B=1,C=1,OUT=1  
# A=1,B=0,C=0,OUT=0  
# A=1,B=0,C=1,OUT=0  
# A=1,B=1,C=0,OUT=1  
# A=1,B=1,C=1,OUT=1
```

+ve edge detector

Design code

```
module pos_edge_detector(input clk,sig,output pe);  
  reg delayed_sig;  
  always@(posedge clk) begin  
    delayed_sig<=sig;  
  end  
  
  assign pe=sig & ~delayed_sig;  
endmodule
```

Simulation results

 


4-bit PISO

Design code

```
module piso(input clk,load,[3:0] data_in,output reg data_out);

    reg [3:0] temp;
always @(posedge clk) begin
    if (load) temp<=data_in;
else begin
    data_out<=temp[3];
    temp <= {temp[2:0],1'b0};
end
end
endmodule
```

Simulation results

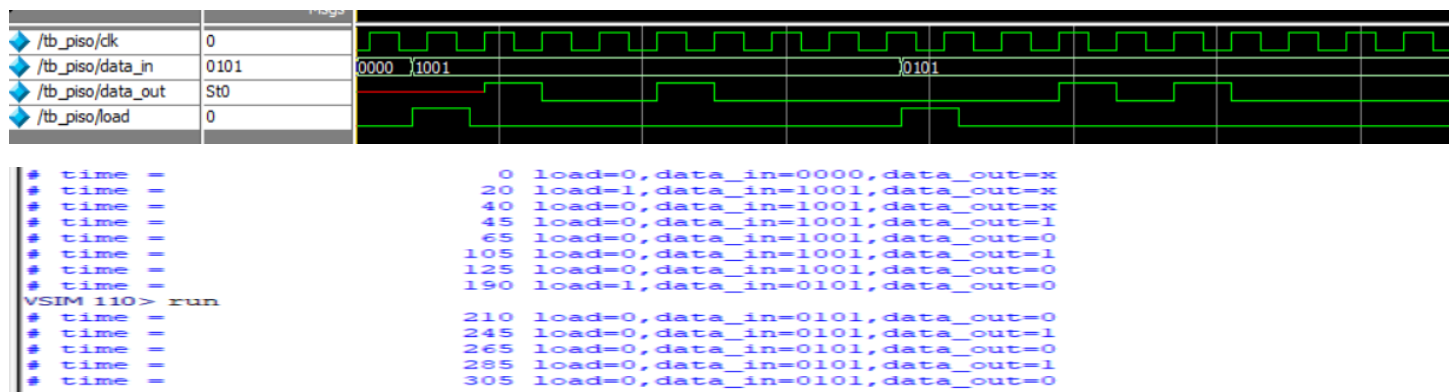

4-bit SIPO


Design code

```
module sipo(input clk,rst,data_in,output [3:0] data_out);
    reg[3:0]temp;
always@(posedge clk)begin
    if(rst) temp<=4'b0000;
else begin
    temp<={temp[2:0],data_in};
end
end
assign data_out=temp;

endmodule
```

Simulation results
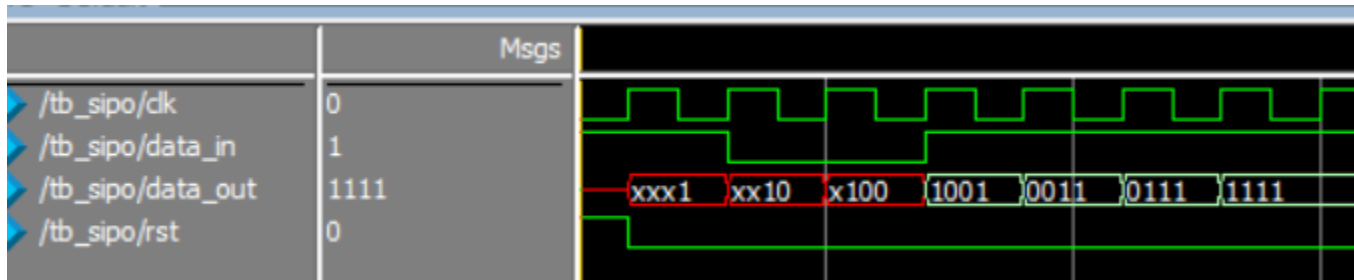
```
# data_in=1,data_out=xxx1
# data_in=0,data_out=xx10
# data_in=0,data_out=x100
# data_in=1,data_out=1001
# data_in=1,data_out=0011
# data_in=1,data_out=0111
# data_in=1,data_out=1111
```



N-BIT RING COUNTER

Design code

```
module D_FF_clr (output reg q,input clk,clr, d);
always @(posedge clk or negedge clr)
if (~clr)
q<= 1'b0;
else
q <= d;

endmodule

module D_FF_pr (output reg q,input clk,pr, d);
always @(posedge clk or negedge pr)
if (~pr)
q<= 1'b1;
else
q <= d;

endmodule


module Ring_Counter#(parameter N = 4)(
input clk,rst,output [N-1:0] q_out );

wire q1;
wire [N-1:0] d,q;

generate
genvar i;
for (i = 0; i < N; i = i + 1) begin
if (i == 0) begin
D_FF_pr u1(q[0],clk,rst,q1);
end
else begin
D_FF_clr u2(q[i],clk,rst,q[i-1]);
end
end
endgenerate
assign q1 = q[N-1];
assign q_out = q;

endmodule
```

Simulation results

 


ROM

Design code

```
module rom #(parameter size=8,parameter filename="rom.txt")
(input clk,rst,[2:0]address,output reg[size-1:0] data);
reg [7:0] rom[0:size-1];
always@(posedge clk or posedge rst) begin
if(rst) begin
$readmemh(filename,rom);
data<='b0;
end
else data<=rom[address];
end
endmodule
```

Simulation results

 


```
VSIM 97> run
# clk=0 ,rst=1address = 0,data = 00
# clk=1 ,rst=0address = 3,data = cc
# clk=0 ,rst=0address = 2,data = cc
# clk=1 ,rst=0address = 2,data = ff
# clk=0 ,rst=0address = 5,data = ff
# clk=1 ,rst=0address = 5,data = 10
```


Memory buffer

Design code

```
module memory_buffer (  
    input  clk,rst,w,r,  
    input  [15:0] data_in,  
    output reg[15:0] data_out);  
    reg [15:0] memory [0:15];  
    reg [3:0] write_ptr,read_ptr = 4'b0000;  
    always @(posedge clk) begin  
        if (rst) begin  
            write_ptr <= 4'b0000;  
            read_ptr <= 4'b0000;  
        end else begin  
            if (w) begin  
                memory[write_ptr] <= data_in;  
                write_ptr <= write_ptr + 1;  
            end  
            if (r) begin  
                data_out <= memory[read_ptr];  
                read_ptr <= read_ptr + 1;  
            end  
        end  
    end  
end  
endmodule
```

Simulation results

 

```
im:/tb_memory_buffer/r \  
im:/tb_memory_buffer/rst  
SIM 93> run  
clk=0 ,rst=1 ,w=x , r=x,data_in = 0000000000000000,data_out = xxxxxxxxxxxxxxxxxxxx  
clk=1 ,rst=1 ,w=x , r=x,data_in = 0000000000000000,data_out = xxxxxxxxxxxxxxxxxxxx  
clk=0 ,rst=0 ,w=1 , r=0,data_in = 0000000000000000,data_out = xxxxxxxxxxxxxxxxxxxx  
clk=1 ,rst=0 ,w=1 , r=0,data_in = 0000000000000000,data_out = xxxxxxxxxxxxxxxxxxxx  
clk=0 ,rst=0 ,w=0 , r=1,data_in = 0000000000000000,data_out = xxxxxxxxxxxxxxxxxxxx  
clk=1 ,rst=0 ,w=0 , r=1,data_in = 0000000000000000,data_out = 0000000000000000  
clk=0 ,rst=0 ,w=1 , r=0,data_in = 1100000000000101,data_out = 0000000000000000  
clk=1 ,rst=0 ,w=1 , r=0,data_in = 1100000000000101,data_out = 0000000000000000  
Break in Module tb_memory_buffer at C:/questasim_10.0b/verilog_lab1/tb_memory_buffer.v line 21  
SIM 94> run  
clk=0 ,rst=0 ,w=0 , r=1,data_in = 1100000000000101,data_out = 0000000000000000  
clk=1 ,rst=0 ,w=0 , r=1,data_in = 1100000000000101,data_out = 1100000000000101  
clk=0 ,rst=0 ,w=0 , r=1,data_in = 1100000000000101,data_out = 1100000000000101
```